Submit your report by Friday, Feb. 10 (please provide screen captures where needed)

Can be written in groups of  $\leq \dim(\mathcal{V}_2 \otimes \mathcal{V}_2)$  – indicate clearly your names on your work!

## Exercise 1

Consider the following quantum circuit:

$$|q_0\rangle$$
  $H$   $|q_1\rangle$ 

- a) Starting from each of the initial basis states  $|00\rangle$ ,  $|01\rangle$ ,  $|10\rangle$ ,  $|11\rangle$ , write the state of the qubits at each step.
- b) Confirm your computations using the IBM Q circuit composer (you can easily prepare the qubits in any of the basis states starting from  $|00\rangle$  and using X gates).
- c) Write down the  $4 \times 4$  matrix corresponding to this circuit and verify that it is unitary.

## Exercise 2


Come up with a 3-qubit circuit that implements  $U_f$ , where f is the boolean function

$$f(x,y) = x OR y.$$


Verify your implementation on IBM Q.
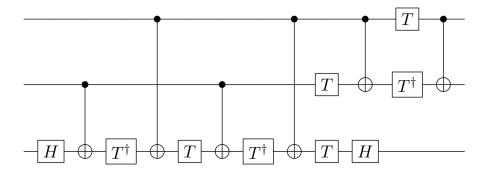
## Exercise 3

Consider the following assemblage U of quantum gates acting on 3 qubits:



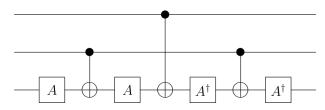- a) Use the IBM Q Vizualizations tab to compute the effect of U on each of the 8 classical states of the system by preparing the 3 qubits accordingly each time.
- b) Verify the above results by hand to make sure you understand what happens; you should now have a matrix representation for U. Do you recognize this gate?
- c) The 3-qubit gate U is sometimes replaced by the following circuit V:



where  $A = R_y(\frac{\pi}{4})$ . By comparing the action of V and U on the qubits, discuss the advantages and inconvenients of using V in place of U.